

SLK	0
BRN	1
RED	2
ORN	3
YEL	4
GRN	5
BLU	6
VLT	7
GRY	8
WHT	9

V^- pin 7 connects to -Sense

V^+ pin 12 connects to V_c pin 11
and then goes to ??

CL (pin 2) goes to ??

CS (pin 3) goes to + output

INV INP (pin 4) goes to R14 R14 = 2.4K
resistor goes to -Sense
2.4K to ground. ~~to ball~~

NI INP (pin 5) to RRBn to pin 6
also goes to capacitor / out V_{ref}
to ~~ground~~ -Sense

V_{ref} (pin 6) goes to 220Ω to NI



pin 8, 9, 10 all connected = V_{out} , V_2 , N_c
goes to power - thingy

pin 11, 12 connected, goes to ?? (see above)


pin 13, 14 = freq comp, goes to cer. disk,
then to pin 4 = INV INP

INV INP also goes to $1/4$ ADJ pot via some
other resistors

BLUBRO Red = 6.1K to pot to +sense

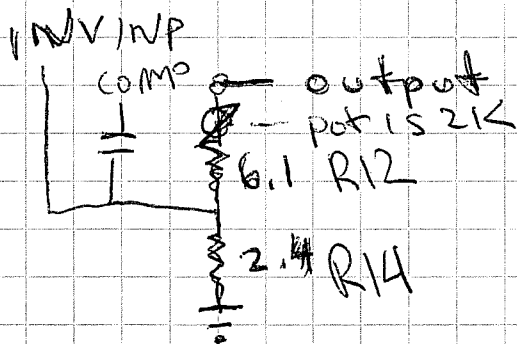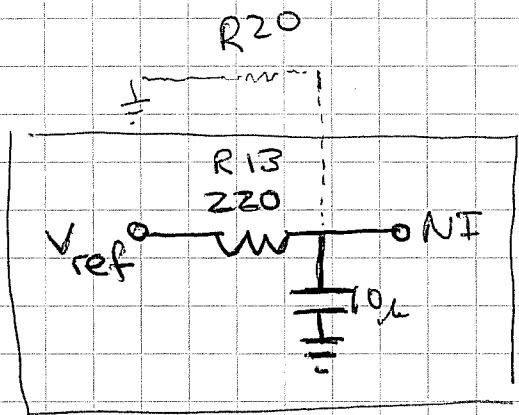

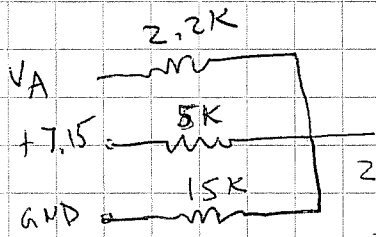if V_A is not connected, then the output will go too high.



if NC, 5.4V
if 0, 2V

$$\frac{0-2}{R} + \frac{7.15-2}{5} + \frac{0-2}{15} = 0$$

$$-\frac{2}{R} + 1.03 - .13 = 0$$

$$\frac{2}{R} = 0.9$$

$$R = 2.2K$$

$$V = IR$$

$$I = \frac{V}{R}$$

at +5V,

$$\frac{5-x}{2.2} + \frac{7-x}{5} + \frac{0-x}{15} = 0$$

$$2.27 - \frac{x}{2.2} + 1.4 - \frac{x}{5} - \frac{x}{15} = 0$$

$$- .45x \quad - .2x \quad - .07x$$

$$3.67 = .72x$$


5.1V = x well, that's close.

control voltage divider:

$$V_A = 0 \rightarrow 5v$$

$$V_+ = 2.04 \rightarrow 5.61v$$

$$V_{out} = 0 \rightarrow 12v$$

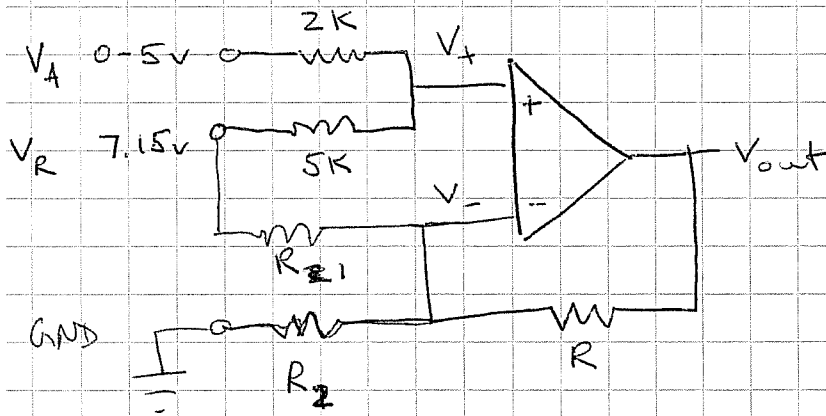

feedback voltage divider:

$$\frac{7.15 - 2.04}{R_1} + \frac{0 - 2.04}{R_2} + 0 - 2.04 = 0$$

$$\frac{5.11}{R_1} - \frac{2.04}{R_2} = 2.04$$

$$\frac{1}{R_1} = 0.40 + \frac{0.40}{R_2}$$

$$\frac{7.15 - 5.61}{R_1} + \frac{0 - 5.61}{R_2} + 12 - 5.61 = 0$$

$$\frac{1.54}{R_1} - \frac{5.61}{R_2} = -6.39$$

$$\frac{1}{R_1} = \frac{3.64}{R_2} - \frac{4.15}{6.39} = 0.40 + \frac{0.40}{R_2}$$

$$\frac{3.24}{R_2} = \frac{4.79}{6.39} = 4.55$$

$$R_2 = 0.71$$

$$R_1 = 1.04$$

$$R = 10k$$

$$R_1 = 10.4k$$

$$R_2 = 7.1k$$

for 0-24v

$$\frac{1}{R_1} = 0.40 + \frac{0.40}{R}$$

$$\frac{7.15-2}{R_1} + \frac{0-2}{R_2} + \frac{0-2}{1} = 0$$

$$\frac{5.15}{R_1} - \frac{2}{R_2} = 2$$

$$\frac{1}{R_1} = 0.39 + \frac{0.39}{R_2}$$

$$\frac{7.15-5}{R_1} + \frac{0-5}{R_2} + \frac{24-5}{1} = 0$$

$$\frac{2.15}{R_1} - \frac{5}{R_2} + 19 = 0$$

$$\frac{1}{R_1} = \frac{2.33}{R_2} - 8.84 = 0.39 + \frac{0.39}{R_2}$$

$$\frac{1.94}{R_2} = 9.23$$

$$R_2 = 0.21$$

$$R_1 = 0.45$$

$$\frac{19}{1} + \frac{2.15}{.45} - \frac{5}{.21} =$$
$$19 + 4.77 - 23.80 = -0.03 \checkmark$$

$$-2 + \frac{5.15}{.45} - \frac{2}{.21} =$$
$$-2 + 11.44 - 9.52 = -0.08 \checkmark$$


if $R_2 = 2.4 \text{ K}$

then need $R_1 = 5.1 \text{ K}$

and $R = 11.4 \text{ K}$

so center value of pot
+ resistor = 11.4K

(~~to~~ V_{ref})

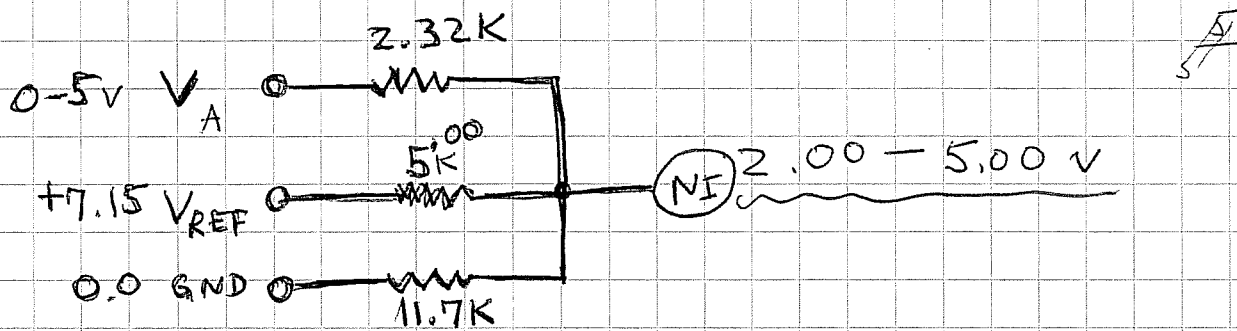


$$\frac{0-2}{R} + \frac{7.15-2}{5} + \frac{0-2}{11.7} = 0$$

$$-\frac{2}{R} + 1.03 - 0.17 = 0$$

$$\frac{2}{R} = .86$$

$$R = 2.32 \text{ K}$$

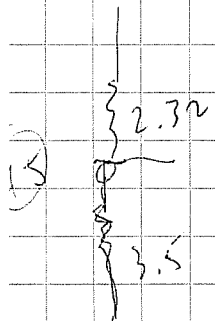

$$\frac{5-x}{2.32} + \frac{7.15-x}{5.00} + \frac{0.0-x}{11.7} = 0$$

$$2.16 - 0.43x + 1.43 - .2x - .09x = 0$$

$$.72x = 3.59$$

$$x = 4.99 \text{ perfect.}$$

1. to test suggest use bench power supply to provide 0 to 5V control.
2. connect +5 to +out and -5 to -out on Power-one.
3. connect -out to ground at bench supply. (for both power supplies!)
4. Replace $220\ \Omega$ R13 with 5.0 K resistor
5. Add 11.7 K resistor at R20
6. Attach 0-5V control voltage through a 2.3 K resistor, at R13 or R20, at end which is next to "R13" or "R20" label.
7. Replace 6.1 K R12 with 10.4 K
8. Attach 5.1 K resistor between other end of R13 (away from "R13" label) and R14, (at the end next to the R14 label).

That's it!

need:
2.3 K
5.0 K
5.1 K (5.0 OK)
11.7 K
10.4 K

For 0-12V

$$\frac{7.15 - 5}{R_1} + \frac{0 - 5}{R_2} + \frac{12 - 5}{1} = 0$$

$$\frac{2.15}{R_1} - \frac{5}{R_2} + 7 = 0$$

$$\frac{1}{R_1} = \frac{2.33}{R_2} - 3.26 = 0.39 + \frac{0.39}{R_2}$$

$$\frac{1.94}{R_2} = 3.65$$

$$R_2 = 0.53$$

$$R_1 = 0.89$$

R14 is Yellow - Purple (?) - Red
= 4.7 K

R12 is Red - Red - Red = 2.2 K pot is 2K

same instructions except

$$R_2 = 4.7 \text{ K}$$

$$R_1 = 7.89 \text{ K}$$

$$R = 8.87 \text{ K} = \underline{\underline{7.9 \text{ K} + 1 \text{ K}}}$$

$$V = IR$$

→ 7. Replace 2.2K R12 with 7.9K

8. Attach 7.9K resistor between
(etc.)

heat tape
5a @ 12V
2.4R

two 4.8R
5a @ 24V

